 


I. Look at the following MUX and its respective truth table. For example, if **sel**='10' then the output is whatever 8 bits that were provided in input **a**. If **sel**='11' then we want the output to be in a high impedance state(Z). Setting up a signal to an high impedance state is obtained with the VHDL command output <= "Z". If you have 8 bits, then you should add the command output <= "ZZZZZZZZ" .



a) Look at the code below and fill in the blanks

b) With active HDL or Xilinx ISE, check the syntax and provide some input/output waveforms. Turn in a printout of the code and a screenshot of the waveforms.

```


library ieee;
use _____;

entity mux is
  port (____, ____: ____ std_logic_vector(7 downto 0);
        sel: in _____;
        ____: out std_logic_vector(7 downto 0));
end mux;

architecture example of _____ is
begin
  process (a, b, sel)
  begin
    if (sel="00") then
      c <= "00000000";
    elsif (_____) then
      c <= a;
    elsif (sel="10") then
      c <= ____;
    else
      c <= "_____";
    end if;
  end ____;
end _____;

```

 2. a) Implement the following function in VHDL using active HDL. Printout the source-code.



a	b	c	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

b) Generate the waveforms for all 8 input combinations using 3 different clocks. Write down the frequency for each clock and take a screenshot of the input/output waveforms. Make sure you press the option zoom-to-fit, so that the entire wave covers a single screen.